

Digital Logic Design 3441 – Spring 2021

Lab #3: The Digital Design Process with SimUAid II

Cody Betzner, Thomas Nguyen

Overview: Goals of the Lab

In this lab we explored a specific boolean function in depth in order to practice performing important algebraic tasks and to become familiar physically constructing these circuits. We performed a minterm expansion and simplified the boolean expression algebraically to get familiar with our assigned function. We also simulated it in SimUAid to verify our findings and confirm that the truth table we obtained matched up with our calculated expectations. We also physically built the circuit to get hands on practice using and implementing the 74LS chips.

Part 1: Minterm Expansion

1. **Unique function:** $BCD + ABCD' + C'D + AB'D$

$$BCD + ABCD' + C'D + AB'D$$

$$(1)BCD + ABCD' + (1)(1)C'D + AB'(1)D \quad \text{operation w/ 1}$$

$$(A+A')BCD + ABCD' + (A+A')(B+B')C'D + AB'(C+C')D \quad \text{op w/ 1}$$

$$ABCD + A'BCD + ABCD' + A(B+B')C'D + A'(B+B')C'D + AB'CD + AB'C'D \quad \text{1st DL}$$

$$ABCD + A'BCD + ABCD' + ABC'D + AB'C'D + A'BC'D + A'B'C'D + AB'CD + AB'C'D \quad \text{1st DL}$$


$$ABCD + A'BCD + ABCD' + ABC'D + AB'C'D + A'BC'D + A'B'C'D + AB'CD \quad \text{Idempotent}$$

$$F(A,B,C,D) = ABCD + A'BCD + ABCD' + ABC'D + AB'C'D + A'BC'D + A'B'C'D + AB'CD$$

2. Our function has 8 minterms.

Part 2: Simplifying your Boolean Function algebraically

LogicAid Minimum SOP

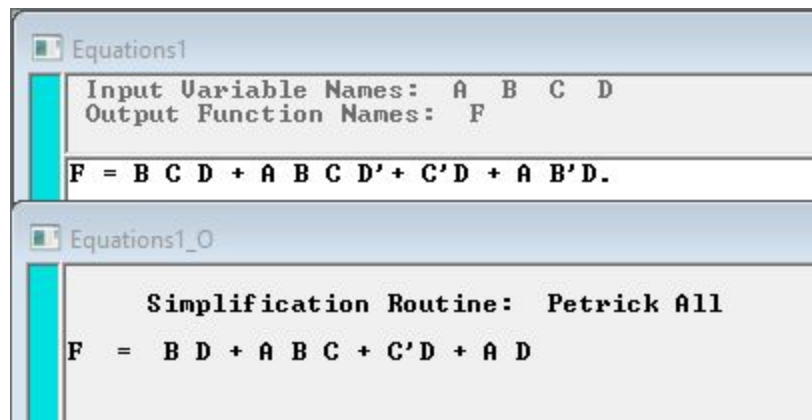

3. Algebraically Simplified SOP

$$\begin{aligned} & BCD + ABCD' + C'D + AB'D \\ & BC(D + AD') + C'D + AB'D \quad \text{1st DL} \\ & BC(D + A) + C'D + AB'D \quad \text{elimination} \\ & BCD + BCA + C'D + AB'D \quad \text{1st DL} \\ & D(BC + C' + AB') + BCA \quad \text{1st DL} \\ & D(B + C' + AB') + BCA \quad \text{elimination} \\ & D(B + A + C') + BCA \quad \text{elimination} \\ & DB + DA + DC' + BCA \quad \text{1st DL} \end{aligned}$$

$$F(A,B,C,D) = ABC + BD + AD + C'D$$

4. The number of input combinations is given by 2^4 for this function. 16 combinations of inputs are needed for this logic circuit.


Part 3: Creating your Boolean function in SimUAid using the clock and input signal

5. Truth Table


Truth_Table13	
Input Variable Names: A B C D	
Output Function Names: F	
0000	0
0001	1
0010	0
0011	0
0100	0
0101	1
0110	0
0111	1
1000	0
1001	1
1010	0
1011	1
1100	0
1101	1
1110	1
1111	1

Truth_Table13_O	
Simplification Routine: PI Chart	
$F = C'D + BD + AD + ABC$	

Circuit Schematic

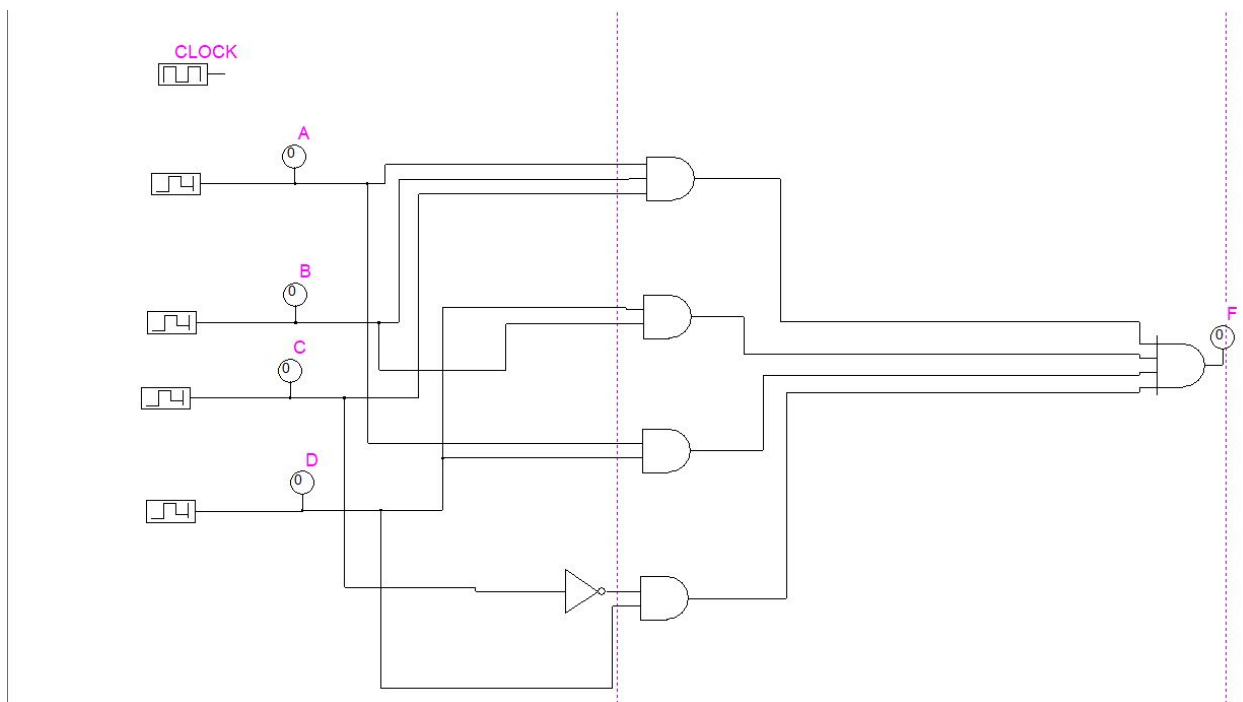

Timing Diagram

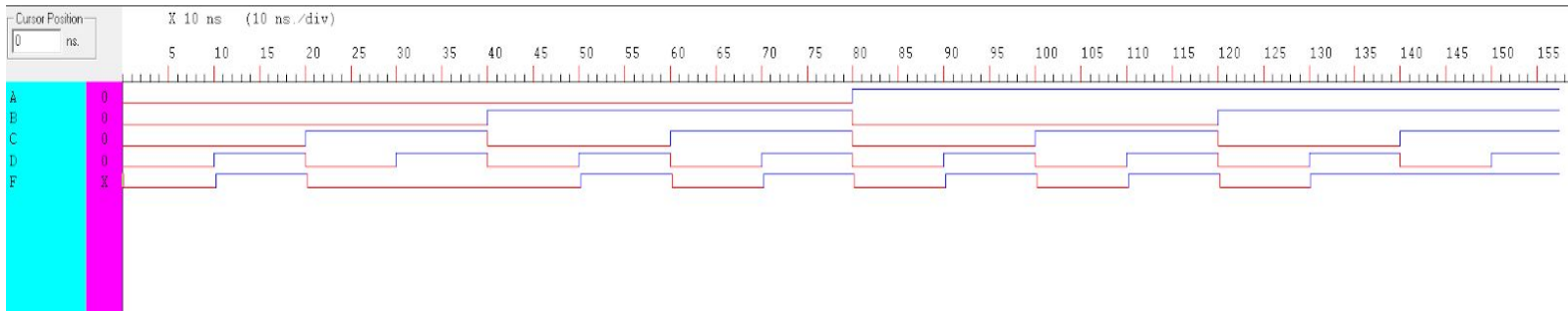

6. Yes, the output matches the truth table.

Part 4: Physically Build your Circuit

Links:

Cody Betzner (UID 1856205)

<https://drive.google.com/file/d/1CqP3ZVnFnUgm9lgb2vd4YaaqGseaApeV/view?usp=sharing>

Thomas Nguyen (UID 1870696)

<https://drive.google.com/file/d/1BpkpbfQ9PfN9MdT8tWhn7ySkQ2VGkxxS/view?usp=sharing>

Conclusion

In this lab we got practice and improved at manipulating logic functions algebraically and simulating them to verify our results. We also physically built a logic function for the first time and learned the importance of things like pull-down resistors and how to troubleshoot our circuits if they do not work correctly.